

## DAFTAR ISI

<b>LEMBAR PERNYATAAN ORISINALITAS .....</b>	<b>i</b>
<b>HALAMAN PENGESAHAN.....</b>	<b>ii</b>
<b>HALAMAN PENGESAHAN PENGUJI .....</b>	<b>iii</b>
<b>KATA PENGANTAR.....</b>	<b>iv</b>
<b>ABSTRAK.....</b>	<b>v</b>
<b>ABSTRACT.....</b>	<b>vi</b>
<b>DAFTAR ISI.....</b>	<b>vii</b>
<b>DAFTAR GAMBAR.....</b>	<b>ix</b>
<b>DAFTAR TABEL .....</b>	<b>x</b>
<b>DAFTAR ISTILAH .....</b>	<b>xi</b>
<b>DAFTAR LAMPIRAN .....</b>	<b>xii</b>
<b>BAB I PENDAHULUAN .....</b>	<b>1</b>
<b>1.1 Latar Belakang .....</b>	<b>1</b>
<b>1.2 Perumusan Masalah .....</b>	<b>2</b>
<b>1.3 Pembatasan Masalah .....</b>	<b>2</b>
<b>1.4 Tujuan Penelitian .....</b>	<b>2</b>
<b>1.5 Manfaat Penelitian .....</b>	<b>2</b>
<b>1.6 Metodologi Penelitian.....</b>	<b>3</b>
<b>1.7 Sistematika Penulisan.....</b>	<b>3</b>
<b>BAB II LANDASAN TEORI .....</b>	<b>4</b>
<b>2.1 Arduino Nano.....</b>	<b>4</b>
<b>2.1.1 Komponen Arduino .....</b>	<b>4</b>
<b>2.1.2 Fungsi Arduino .....</b>	<b>5</b>
<b>2.1.3 Jenis-Jenis Arduino.....</b>	<b>5</b>
<b>2.2 Pemrograman .....</b>	<b>6</b>
<b>2.3 Relay 4 Channel 5 Volt .....</b>	<b>8</b>
<b>2.3.1 Skmema Relay 5 Volt.....</b>	<b>9</b>
<b>2.3.2 Jenis-Jenis Relay .....</b>	<b>9</b>
<b>2.4 Project Mini Board.....</b>	<b>10</b>
<b>2.4.1 Jenis-Jenis Breadboard .....</b>	<b>11</b>

<b>2.5 Modul Breadboard Power Supply MB-102.....</b>	<b>12</b>
<b>2.6 Modul Bluetooth HC-05.....</b>	<b>13</b>
<b>2.6.1 Spesifikasi Modul Bluetooth HC-05 .....</b>	<b>14</b>
<b>2.6.2 Kode Perintah Bluetooth HC-05 .....</b>	<b>15</b>
<b>2.7 Kabel Jumper .....</b>	<b>15</b>
<b>2.7.1 Jenis-Jenis Kabel Jumper .....</b>	<b>15</b>
<b>2.8 Adaptor 12 Volt.....</b>	<b>16</b>
<b>2.8.1 Komponen Adaptor .....</b>	<b>17</b>
<b>2.9 Kabel USB .....</b>	<b>18</b>
<b>BAB III PERANCANGAN ALAT.....</b>	<b>22</b>
<b>3.1 Perancangan Sistem.....</b>	<b>22</b>
<b>3.2 Perancangan Perangkat Lunak.....</b>	<b>22</b>
<b>3.3 Perancangan Alat .....</b>	<b>23</b>
<b>BAB IV ANALISA PENGUKURAN.....</b>	<b>26</b>
<b>4.1 Analisa Alat Pengujian .....</b>	<b>26</b>
<b>4.1.1 Hasil Pengujian Tegangan Adaptor 12 Volt .....</b>	<b>27</b>
<b>4.1.2 Hasil Pengujian Tegangan Arduino Nano .....</b>	<b>28</b>
<b>4.1.3 Hasil Pengujian Tegangan Relay 4 Channel 5 Volt.....</b>	<b>29</b>
<b>4.1.4 Hasil Pengujian Tegangan Bluetooth HC-05.....</b>	<b>30</b>
<b>4.1.5 Hasil Pengujian Tegangan Lampu .....</b>	<b>31</b>
<b>4.1.6 Hasil Pengujian Tegangan Stop Kontak.....</b>	<b>32</b>
<b>4.2 Analisa Pengujian Software.....</b>	<b>33</b>
<b>4.3 Pengujian Koneksi Jarak Tanpa Halangan .....</b>	<b>38</b>
<b>4.4 Pengujian Koneksi Jarak Dengan Adanya Halangan .....</b>	<b>39</b>
<b>BAB V PENUTUP .....</b>	<b>41</b>
<b>5.5 Kesimpulan .....</b>	<b>41</b>
<b>5.6 Saran.....</b>	<b>41</b>
<b>DAFTAR PUSTAKA .....</b>	<b>42</b>
<b>LAMPIRAN.....</b>	<b>43</b>